



香港科技大學
THE HONG KONG UNIVERSITY OF SCIENCE AND TECHNOLOGY

ELEC 3310

Digital Fundamentals and System Design

Wenchao Miao

Outline Lecture 1 Introductory Concepts



THE HONG KONG
UNIVERSITY OF SCIENCE
AND TECHNOLOGY

1 Basic Concepts

2 Digital vs. Analog

3 Digital Representation

4 Logic Design

5 Boolean Algebra


Main Content

1. Basic Concepts of Digital Fundamentals and System Design
2. Learning Outcomes

 1. Digital Fundamentals and System Design




Why learning Digital Fundamentals and System Design is important ?

Digital systems form the **backbone** of modern technology—from **smartphones** and **computers** to advanced **robotics**, **AI**, and **IoT** devices. This course provides the essential foundation for designing and understanding these systems, making it crucial for future engineers and computer scientists



   (1) Core Knowledge for Hardware & Embedded Systems





- Digital logic is the basis of microprocessors, FPGAs, and embedded systems
- Understanding how logic gates, registers, and state machines work is essential for designing efficient hardware
- Many industries (automotive, aerospace, consumer electronics) rely on digital systems



1. Basic Concepts

    (2) Bridging Software and Hardware



- Modern computing requires hardware-software co-design (e.g., optimizing algorithms for FPGAs)
- Learning Hardware Description Languages (HDLs) like Verilog/VHDL helps you write code that directly controls hardware



  (3) Foundation for Advanced Computing

Concepts from this course are used in:

- Computer Architecture(CPU design, memory systems)
- Robotics & Control Systems(sensor interfacing, motor control)
- AI & Machine Learning(accelerators, custom ASICs/FPGAs for deep learning)



(4) Hands-On Problem-Solving Skills

- We' ll design and simulate real digital circuits
- Work with FPGA boards (used in industries for prototyping)
- Debug and optimize circuits—skills highly valued in R&D and electronics design

(5) Career Opportunities

- VLSI (Chip Design) Engineer– Design processors at **Intel, AMD, NVIDIA**
- Embedded Systems Engineer– Work on **IoT, automotive** systems
- FPGA Developer– Used in **telecom, defense, and AI** acceleration
- Hardware Security Engineer– Protect systems from **cyber threats**

**Whether you're into AI, robotics, chip design, or IoT, mastering digital logic is a must
This course isn't just about theory—it's about building real systems that power the technology
of tomorrow**

2. Learning Outcomes

1. **Explain the basic differences between digital and analog quantities**
2. **Show how voltage levels are used to represent digital quantities**
3. **Describe various parameters of a pulse waveform such as rise time, fall time, pulse width, frequency, period, and duty cycle**
4. **Explain the basic logic functions of NOT, AND, and OR**
5. **Describe several types of logic operations and explain their application in an example system**
6. **Describe the basic laws and rules of Boolean algebra**
7. **Apply DeMorgan's theorems to Boolean expressions**

Main Content

Digital vs. Analog: Principles and Advantages

1. Core Definitions
2. Real-World Comparisons

2. Digital vs. Analog

(1) Analog (Continuous) vs. Digital (Discrete) Signals

- Analog signal – continuous values (infinite possibilities)
- Digital signal – discrete values (finite set of values)



Discrete values



Continuous values



Secure Digital Card
(SD Card)




Cassette Tape

- Digital data can be processed and transmitted more efficiently and reliably than analog data
- Digital data storage has a great advantage. Music can be stored more compactly and reproduced with greater accuracy and clarity in digital form than possible in analog form
- Noise (unwanted voltage fluctuations) does not affect digital data nearly as much as it does analog signals

2. Digital vs. Analog

 (2) Quantization & Digitization of Analog Data




Discrete values



Continuous values

 Sampled-value representation (quantization) of the analog quantity. Each value represented by a dot can be digitized by representing it as a digital code that consists of a series of 1s and 0 s.




digitized

10110011101

2. Real-World Comparisons

 
(1) Analog vs. Digital Audio Systems (Microphone vs. CD Player)



2. Real-World Comparisons

(1) Analog vs. Digital Audio Systems (Microphone vs. CD Player)


A basic diagram for a CD player system

 


2. Real-World Comparisons

 (2) Hybrid Systems in Mechatronics (Robotic Arm Example)

Both analog and digital systems are used in Mechatronics (robotic systems)



(b) Robotic arm

 


(c) Automotive assembly line

(a) Mechatronic system block diagram

2. Real-World Comparisons

 (3) Digital Circuitry in Modern Hardware (Intel Processor Example)

How a digital circuit looks under a microscope



5 GHz 10th Gen Intel® Core™ H-series mobile processors

Main Content

Digital Representation: Logic Levels & Waveform Characteristics

1. Logic Standards
2. Pulse and Waveform Analysis
3. Synchronization
4. Data Transfer

1. Logic Standards


(1) Logic Levels (HIGH/LOW, Positive/Negative Logic)

1. Only two possible levels (states) exist in digital circuits
 - HIGH Voltage and LOW Voltage (Logic levels)
2. Hence, the circuit behavior is described by a binary system
 - Positive logic: “1” for HIGH Voltage and “0” for LOW Voltage
 - Negative logic: “1” for LOW Voltage and “0” for HIGH Voltage
 - A binary digit is called “bit” – bit 0; bit 1
 - Combinations of 1s and 0s form “digital codes” or “codes”
3. We use decimal system in daily life because of our 10 fingers

3. Digital Representation

(2) Valid Logic-Level Voltage Ranges

Voltage (Logic) Levels

 


3. Digital Representation


2. Pulse and Waveform Analysis

(1) Ideal Pulse Parameters (Rising/Falling Edges)

Logic Pulses

 

(a) Positive-going pulse

 


(b) Negative-going pulse

3. Digital Representation

 (2) Digital Waveforms as Binary Data (Pulse Trains)

Most waveforms in digital systems are composed of series of pulses (pulse trains)


A digital waveform carries binary information



10100010111101000010111101000101011110101001010
10001010111010101010001010100010101001110100010
10100010111101010001010111010101000010101110101
00010101001001111010101000101010101110101010001
01010100111101010100010101010101010001010101000
11101010000101001010010111010001001010101001011


3. Digital Representation

 (3) Non-Ideal Pulse Distortions (Rise Time, Ringing, Droop)




3. Digital Representation

(4) Oscilloscope Measurement

 

 (5) Periodic vs. Aperiodic Signal Classification

Periodic pulse waveform (repeats itself at a fixed time interval called period)



Period = $T_1 = T_2 = T_3 = \dots = T_n$ **Unit in seconds**

Frequency = $\frac{1}{T}$ **Unit in Hertz (number of pulses per second)**


Aperiodic (or non-periodic) pulse waveform



 (6) Duty Cycle Calculation

- An important characteristic of a **periodic** digital waveform
- The ratio of the pulse width (t_W) to the period (T)
- Expressed as a percentage


$$\text{Duty cycle} = \left(\frac{t_W}{T} \right) \times 100 \%$$



3. Synchronization

 (1) Timing Diagrams (Multi-Signal Synchronization)


A timing diagram is a graph of digital waveforms showing the actual time relationship of two or more waveforms and how each waveform changes in relation to the others



 (2) Clock Signals (Bit Time and System Synchronization)

- The Clock – basic timing waveform reference to all other waveforms
- The clock is a periodic waveform and thus **carries no information** itself
- Each interval between clock pulses (the period) equals the time for one bit
- Utilized to synchronize all other waveforms in a digital system (sequential logic)

Each bit in a sequence occupies a defined time interval called a bit time



Each change in level of waveform A occurs at the leading edge of the clock

3. Digital Representation

4. Data Transfer


Illustration of serial and parallel transfer of binary data
Only the data lines are shown

A byte contains eight bits

A group of several bits can contain binary information, such as a number or a letter.

Serial transfer: sends one bit at a time over a single line

 
Takes longer time (eight clock cycles for a byte)



 (a) Serial transfer of 8 bits of binary data. Interval t_0 to t_1 is first.

Parallel transfer: sends multiple bits at once over multiple lines (bus)

All bits being transferred in one clock cycle



(b) Parallel transfer of 8 bits of binary data. The beginning time is t_0 .


Main Content

Logic Design: Core Gates and Functional Blocks



1. Basic Gates
2. Derived Gates
3. Combinational and Sequential Logic Function

 1. Basic Gates-(1) AND, OR, NOT

A circuit that performs a specified logic function (AND, OR) is called a **LOGIC GATE**.








NOT

  




The lines connected to each symbol are the inputs and outputs. The inputs are on the left of each symbol and the output is on the right.



AND

     

OR

   


1. Basic Gates-(2) Logic Operations Overview

- Any logic function can be implemented by combining a number of basic logic functions (AND, OR, NOT) in a specific arrangement (the design).
- Examples: comparison, arithmetic, code conversion, encoding, decoding, and data selection, distribution, counting, and storage.
- A digital system contains circuits performing individual logic functions being connected to perform a specified operation or produce a desired output.

2. Derived Gates

(1) Basic Gate

 

NOT

$$X = \overline{A}$$

TABLE 3-1


Inverter truth table.

Input	Output
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

Alternative Symbol

$$X = A'$$

N-input AND Gate

 

N AND


TABLE 3-2

Truth table for a 2-input AND gate. $X = AB$

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1

1 = HIGH, 0 = LOW

N-input OR Gate

 

N OR


TABLE 3-5

Truth table for a 2-input OR gate. $X = A + B$

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	1

1 = HIGH, 0 = LOW




(2) NAND

 


(a) Distinctive shape, 2-input NAND gate and its NOT/AND equivalent

Inputs		Output
A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

1 = HIGH, 0 = LOW.

   

(3) NOR




 


(a) Distinctive shape, 2-input NOR gate and its NOT/OR equivalent


$$X = \overline{A + B}$$

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

1 = HIGH, 0 = LOW.

 
 
 
 


(4) XOR

 


$$X = A \oplus B$$

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

 
 
 
 


(5) XNOR

 

$$X = \overline{A \oplus B}$$

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

    


3.1 Combinational Logic Functions


(1) Comparator

Performs magnitude comparison of two binary numbers and provides the result by producing HIGH at the corresponding output. The other two outputs remain LOW

 Example: comparing binary codes for 2 and 5



(a) Basic magnitude comparator

 


(b) Example: A is less than B ($2 < 5$) as indicated by the HIGH output ($A < B$)


(2) Adder

Performs addition of two binary numbers along with a carry input (single bit) and provides the result at the sum Σ and carry output

 Example: adding binary codes 3 and 9 with a carry input bit 0. The result 12 is generated at the outputs




(a) Basic adder

 

(b) Example: A plus B ($3 + 9 = 12$)

 
(3) Encoder

9 in base 10 = 1001 in base 2
 $(9)_{10} = (1001)_2$



 (4) Decoder

A decoder used to convert a special binary code into a 7-segment decimal readout




Interfacing digital circuits to outside world

(5) Multiplexer/Demultiplexer

Both are electronic switches and perform data selection/distribution logic functions

**Multiplexer switches
many inputs to one output**

 **Demultiplexer switches
one input to many outputs**



3.2 Sequential Logic Functions

(1) 4-bit Serial Shift Register (Bit-by-Bit Loading)

Register = Memory

Shift because data is loaded by shifting bits

Example of the operation of a 4-bit serial shift register Each block represents one storage "cell" called flip-flop

Serial bits
on input line

0101 →



Initially, the register contains only *invalid* data or all zeros as shown here.

010 →




First bit (1) is shifted serially into the register.

01 →




Second bit (0) is shifted serially into register and first bit is shifted right.

0 →

 

Third bit (1) is shifted into register and the first and second bits are shifted right.

→

 


Fourth bit (0) is shifted into register and the first, second, and third bits are shifted right. The register now stores all four bits and is full.

(2) 4-bit Parallel Register (Simultaneous Data Loading)


Parallel because all bits are loaded at once (in parallel)

Example of the operation of a 4-bit parallel shift register

Parallel bits
on input lines

 

 Initially, the register is empty,
containing only nondata zeros.




All bits are shifted in and
stored simultaneously.

(3) Counters (Event Tracking with Binary Codes)


Counters are special type registers with additional logic circuits

Illustration of basic counter operation

 

Applied Digital Systems

 Block diagram of a tablet-bottling system



Main Content


Boolean Algebra: Laws and Simplification Techniques

1. Foundational Operations
2. Algebraic Laws
3. Simplification Techniques

1. Foundational Operations


(1) Boolean Addition (OR) and Multiplication (AND)

Boolean Addition (OR operation)

 

“+” means OR
operation
(not a binary
addition)

Boolean Multiplication (AND operation)

 



“•” means AND
operation
(not a binary
multiplication)

2. Algebraic Laws

- **Commutative Laws**
- **Associative Laws**
- **Distributive Laws**

5. Boolean Algebra


(1) Commutative Laws

  

5. Boolean Algebra




(2) Associative Laws

 


5. Boolean Algebra


(3) Distributive Laws

 


$$X = A(B + C)$$

 

$$X = AB + AC$$

 

$$X = A + BC$$

 

$$X = (A + B)(A + C)$$

1. Simplification Techniques

(1) Boolean Rules

Basic rules of Boolean algebra.

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\bar{\bar{A}} = A$

10. $A + AB = A$

11. $A + \bar{A}B = A + B$


12. $(A + B)(A + C) = A + BC$

A , B , or C can represent a single variable or a combination of variables.

 (2) DeMorgan's Theorems

The complement of two or more ANDed variables is equivalent to the OR of the complements of the individual variables


$$\overline{XY} = \overline{X} + \overline{Y}$$



Inputs		Output	
X	Y	$\overline{XY}$	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

The complement of two or more ORed variables is equivalent to the AND of the complements of the individual variables
 
$$\overline{X + Y} = \overline{X} \overline{Y}$$



Inputs		Output	
X	Y	$\overline{X + Y}$	$\overline{X} \overline{Y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

(2) DeMorgan's Theorems

Applying DeMorgan's Theorems

The following procedure illustrates the application of DeMorgan's theorems and Boolean algebra to the specific expression

$$\overline{\overline{A + BC + D(E + F)}}$$

Step 1: Identify the terms to which you can apply DeMorgan's theorems, and think of each term as a single variable. Let $\overline{A + BC} = X$ and $\overline{D(E + F)} = Y$.

Step 2: Since $\overline{X + Y} = \overline{X} \overline{Y}$,

$$\overline{\overline{A + BC} + \overline{D(E + F)}} = \overline{\overline{A + BC}} \overline{\overline{D(E + F)}}$$

Step 3: Use rule 9 ($\overline{\overline{A}} = A$) to cancel the double bars over the left term (this is not part of DeMorgan's theorem).

$$\overline{\overline{A + BC}} \overline{\overline{D(E + F)}} = (A + BC) \overline{\overline{D(E + F)}}$$

Step 4: Apply DeMorgan's theorem to the second term.

$$(A + BC) \overline{\overline{D(E + F)}} = (A + BC) (\overline{\overline{D}} + \overline{\overline{E + F}})$$

Step 5: Use rule 9 ($\overline{\overline{A}} = A$) to cancel the double bars over the $E + F$ part of the term.

$$(A + BC) (\overline{\overline{D}} + \overline{\overline{E + F}}) = (A + BC) (\overline{D} + E + F)$$



香港科技大學
THE HONG KONG UNIVERSITY OF SCIENCE AND TECHNOLOGY

Thank you for listening !

