



香港科技大學
THE HONG KONG UNIVERSITY OF SCIENCE AND TECHNOLOGY

ELEC 3310

Digital Fundamentals and System Design

Wenchao Miao

Outline Lecture 13 Finite State Machines, Further Examples




THE HONG KONG
UNIVERSITY OF SCIENCE
AND TECHNOLOGY

1 Vending Machine

2 Moore and Mealy Machines

3 Latch and FF

- **Project Specifications**
 - Deliver a package of gum after 15 cents are deposited
 - Single coin slot for dimes (10 cents), nickels (5 cents)
 - Keep the change
 - More features are possible:
 - » out-of-gum condition, make change, accept quarters (25 cents) or dollars, choice of gum,
- **Understand the Specifications**
 - With a block diagram
 - 2 data inputs
 - 1 clock input
 - 1 open output
 - 1 reset input
 - » initial state

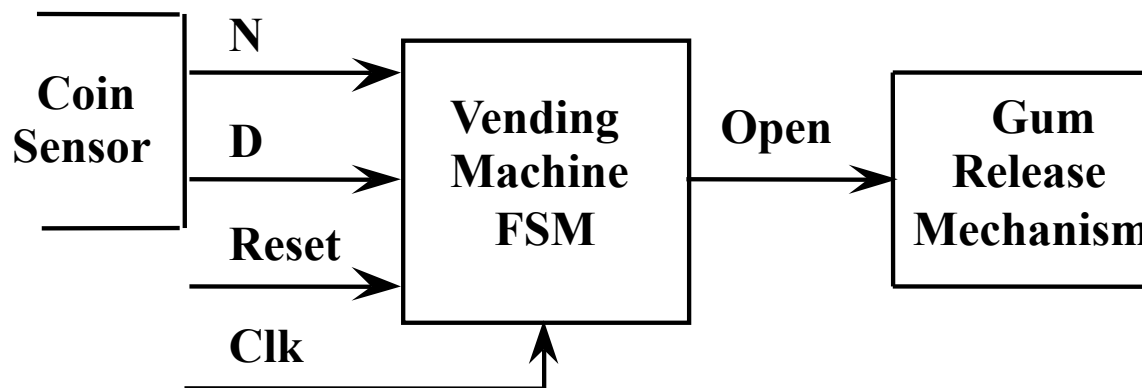

- Suitable Abstract Representation

- Tabulate typical input sequences:


- 3 nickels
- nickel, dime
- dime, nickel
- two dimes

- Draw state diagram:

- Inputs: N, D, reset
- Output: open chute

- Assumptions:

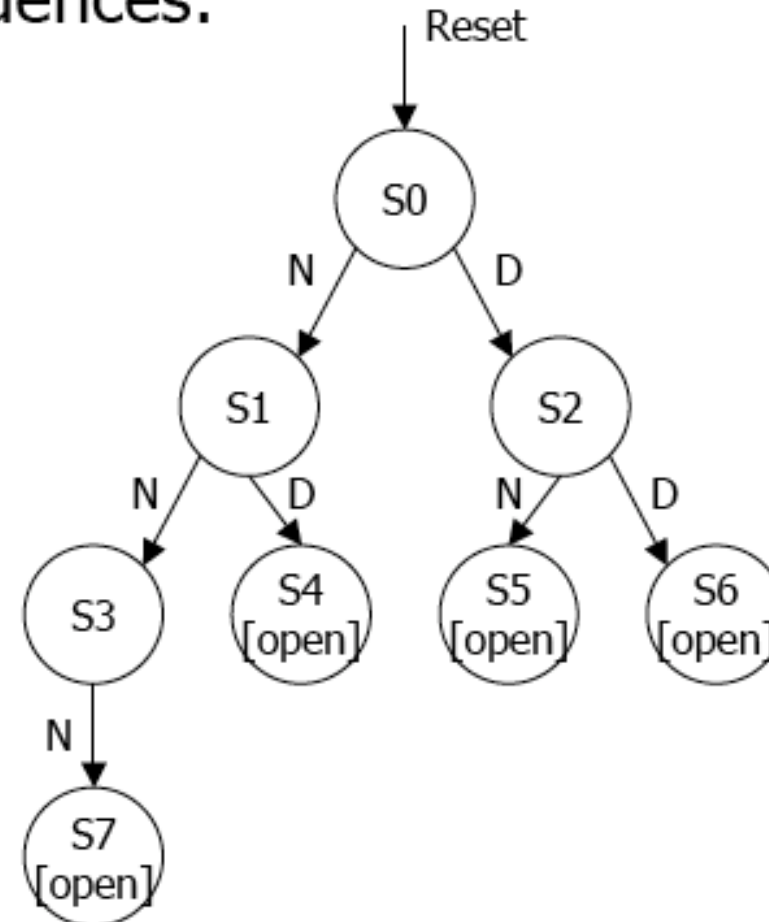
- Assume N and D asserted for one cycle
- Each state has a self loop for $N = D = 0$ (no coin)



Draw minimized state diagram


- **Two FSM are equivalent if they produce the same output sequences given the same input sequences.**
- **The internal 'states' are not relevant from the observer point of view**
- **Hence, for a given state machine we can try to find an equivalent state machine, with fewer internal states (i.e. simpler? fewer flip-flops? perhaps...)**
- **The principle of FSM state reduction is based on *identifying and merging* equivalent states.**
- **"Two internal states are said to be equivalent if for each input combination they give exactly the same output and send the circuit to either the same state or to an equivalent state"**

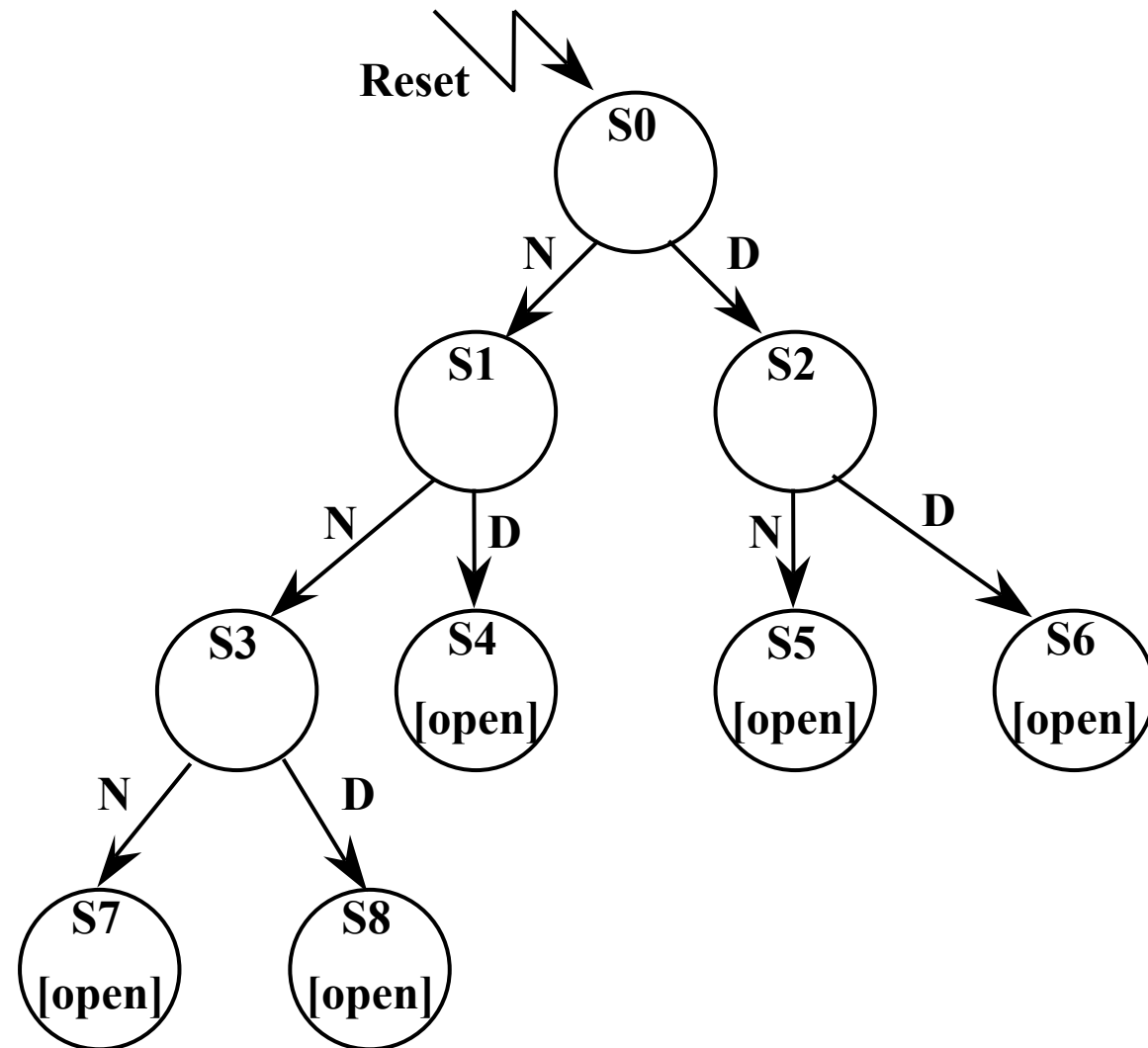- **Perform state reduction**
 - **Equivalent states can be merged**
 - » Same output
 - » Same state transitions
 - **S4, S5, S6, S7, S8 are equivalent**
 - » Same output [open]
 - » Same state transitions
 - reset to S0
 - **S2 and S3 are equivalent**
 - » Same output
 - » Same state transitions
 - **4 states**
 - » S0 (0¢)
 - » S1 (5¢)
 - » S2' (10¢)
 - » S4' (15¢, open)



Vending Machine - State Reduction

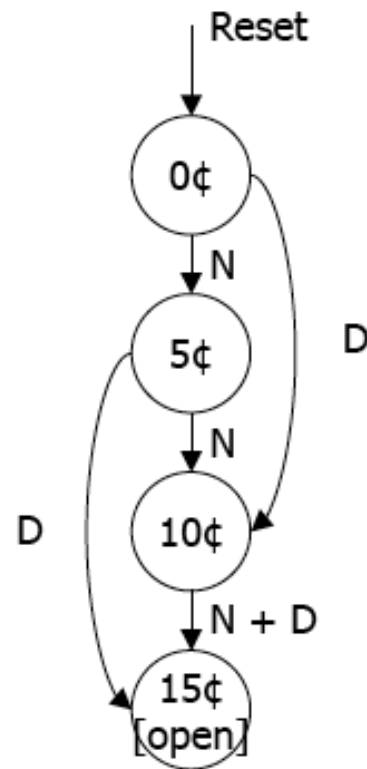- Perform state reduction
 - Minimized state-transition diagram and table
 - (11) is not a possible input, don't care
 - » since two coins cannot be inserted at the same time



present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

symbolic state table

Vending Machine - State Assignment

- Perform state assignment
 - Assign binary values to the states
 - 4 states
 - » 2 flip-flops
 - State assignment
 - » 0 ¢ by 00
 - » 5 ¢ by 01
 - » 10 ¢ by 10
 - » 15 ¢ by 11
- Choose D flip-flop
 - $D \rightarrow Q^+$

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	–	–	–
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	–	–	–
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	–	–	–
1	1	0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1
		1	1	–	–	–

Vending Machine - Implementation

DN	Q ₁ Q ₀			
	00	01	11	10
00	0	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	1	1

K-map for D₁

$$D_1 = Q_1 + D + Q_0 N$$

DN	Q ₁ Q ₀			
	00	01	11	10
00	0	1	1	0
01	1	0	1	1
11	X	X	X	X
10	0	1	1	1

$$D_0 = NQ_0' + Q_0N' + Q_1N + Q_1D$$

DN	Q ₁ Q ₀			
	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	X	X	X	X
10	0	0	1	0


K-map for Open

$$OPEN = Q_1 Q_0$$

Vending Machine - Implementation



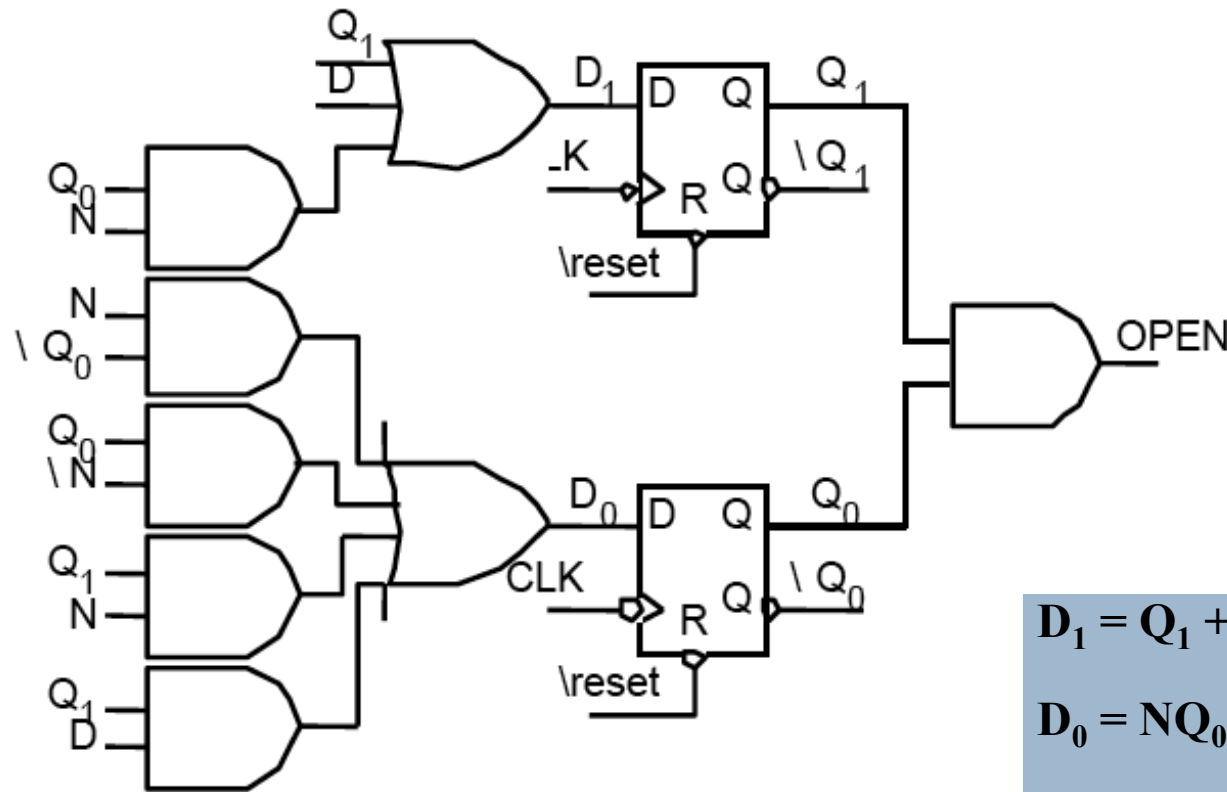THE HONG KONG
UNIVERSITY OF SCIENCE
AND TECHNOLOGY



$$D_1 = Q_1 + D + Q_0 N$$

$$D_0 = NQ_0' + Q_0N' + Q_1N + Q_1D$$

$$OPEN = Q_1 Q_0$$

Vending Machine – Implementation (JKFF)



Present State		Inputs		Next State		J_1	K_1	J_0	K_0
Q_1	Q_0	D	N	Q_1^+	Q_0^+				
0	0	0	0	0	0	0	X	0	X
		0	1	0	1	0	X	1	X
		1	0	1	0	1	X	0	X
		1	1	X	X	X	X	X	X
0	1	0	0	0	1	0	X	X	0
		0	1	1	0	1	X	X	1
		1	0	1	1	1	X	X	0
		1	1	X	X	X	X	X	X
1	0	0	0	1	0	X	0	0	X
		0	1	1	1	X	0	1	X
		1	0	1	1	X	0	1	X
		1	1	X	X	X	X	X	X
1	1	0	0	1	1	X	0	X	0
		0	1	1	1	X	0	X	0
		1	0	1	1	X	0	X	0
		1	1	X	X	X	X	X	X

Q	Q+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Vending Machine – Implementation (JKFF)

Present State		Inputs		Next State		J_1	K_1	J_0	K_0
Q_1	Q_0	D	N	Q_1^+	Q_0^+				
0	0	0	0	0	0	0	X	0	X
		0	1	0	1	0	X	1	X
		1	0	1	0	1	X	0	X
		1	1	X	X	X	X	X	X
0	1	0	0	0	1	0	X	X	0
		0	1	1	0	1	X	X	1
		1	0	1	1	1	X	X	0
		1	1	X	X	X	X	X	X
1	0	0	0	1	0	X	0	0	X
		0	1	1	1	X	0	1	X
		1	0	1	1	X	0	1	X
		1	1	X	X	X	X	X	X
1	1	0	0	1	1	X	0	X	0
		0	1	1	1	X	0	X	0
		1	0	1	1	X	0	X	0
		1	1	X	X	X	X	X	X

$K\text{-map for } J_1$

Q_1Q_0	00	01	11	10
DN				
00	0	0	X	X
01	0	1	X	X
11	X	X	X	X
10	1	1	X	X

$$J_1 = D + Q_0 N$$

$K\text{-map for } K_1$

Q_1Q_0	00	01	11	10
DN				
00	X	X	0	0
01	X	X	0	0
11	X	X	X	X
10	X	X	0	0

$$K_1 = 0$$

Vending Machine – Implementation (JKFF)



Present State		Inputs		Next State		J_1	K_1	J_0	K_0
Q_1	Q_0	D	N	Q_1^+	Q_0^+				
0	0	0	0	0	0	0	X	0	X
		0	1	0	1	0	X	1	X
		1	0	1	0	1	X	0	X
		1	1	X	X	X	X	X	X
0	1	0	0	0	1	0	X	X	0
		0	1	1	0	1	X	X	1
		1	0	1	1	1	X	X	0
		1	1	X	X	X	X	X	X
1	0	0	0	1	0	X	0	0	X
		0	1	1	1	X	0	1	X
		1	0	1	1	X	0	1	X
		1	1	X	X	X	X	X	X
1	1	0	0	1	1	X	0	X	0
		0	1	1	1	X	0	X	0
		1	0	1	1	X	0	X	0
		1	1	X	X	X	X	X	X

$Q_1 Q_0$ *K-map for J_0*

	00	01	11	10
DN				
00	0	X	X	0
01	1	X	X	1
11	X	X	X	X
10	0	X	X	1

$$J_0 = N + Q_1 D$$

$Q_1 Q_0$ *K-map for K_0*

	00	01	11	10
DN				
00	X	0	0	X
01	X	1	0	X
11	X	X	X	X
10	X	0	0	X

$$K_0 = Q_1' N$$

Vending Machine – Implementation (JKFF)




THE HONG KONG
UNIVERSITY OF SCIENCE
AND TECHNOLOGY

$$J_1 = D + Q_0 N$$


$$K_1 = 0$$

$$J_0 = N + Q_1 D$$


$$K_0 = Q'_1 N$$

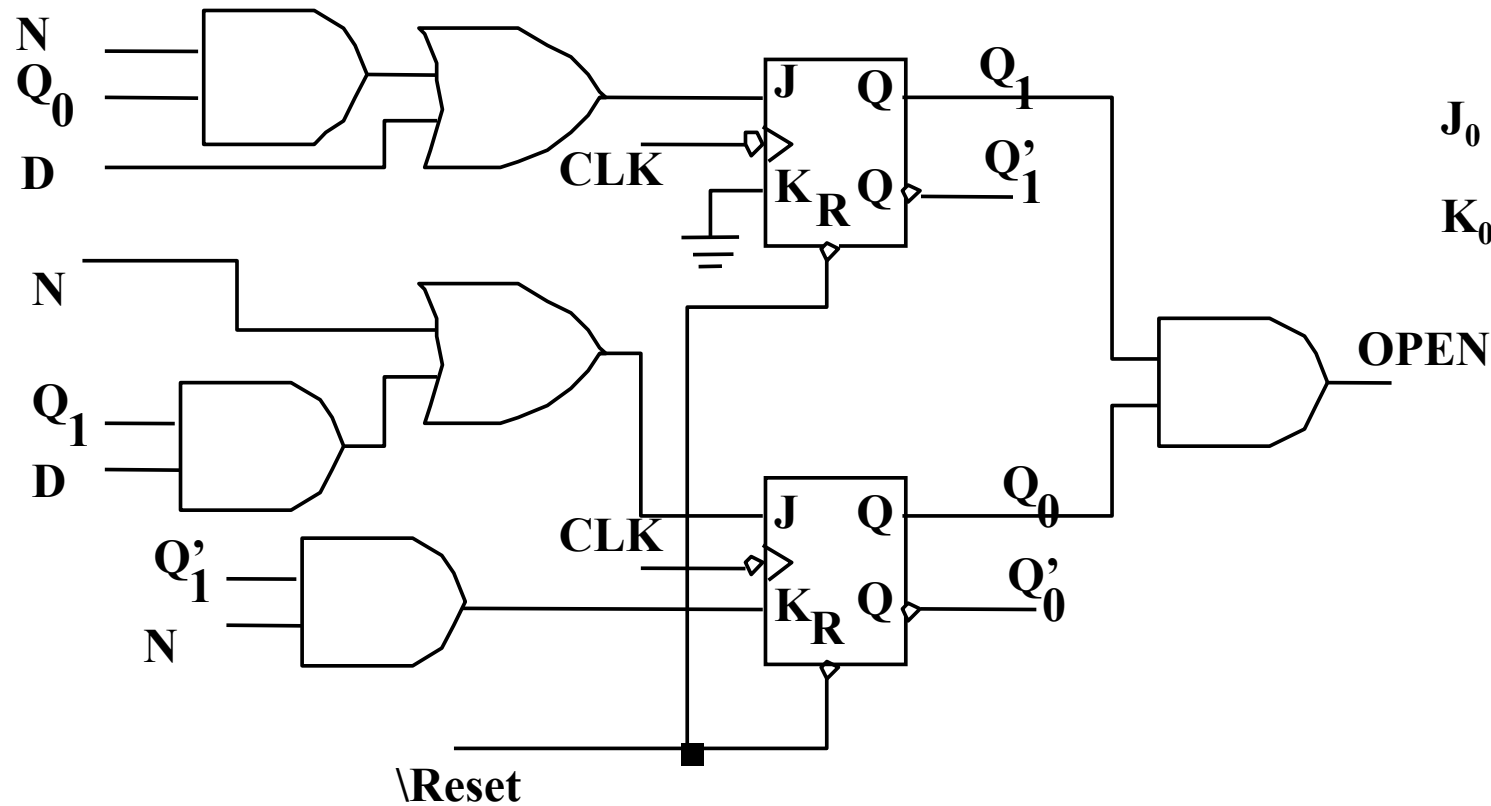

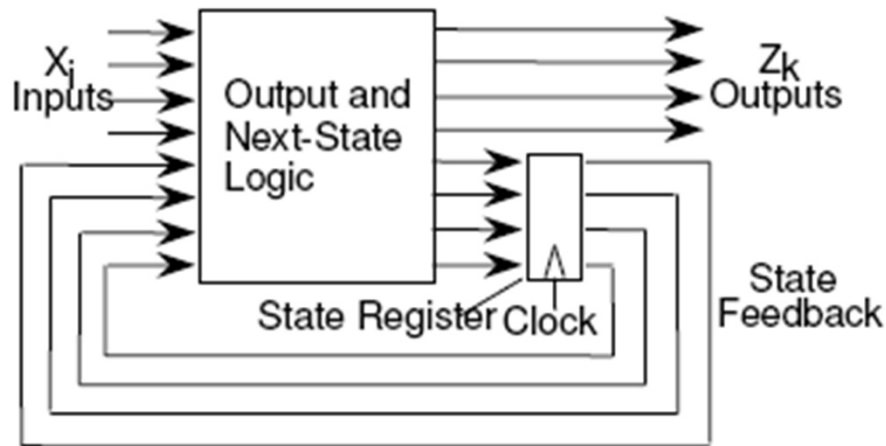- **Moore Machine**
 - Outputs are function solely of the current state
 - Outputs change synchronously with state changes
- **Mealy Machine**
 - Outputs depend on state AND inputs
 - Input change causes an immediate output change





Mealy Machine

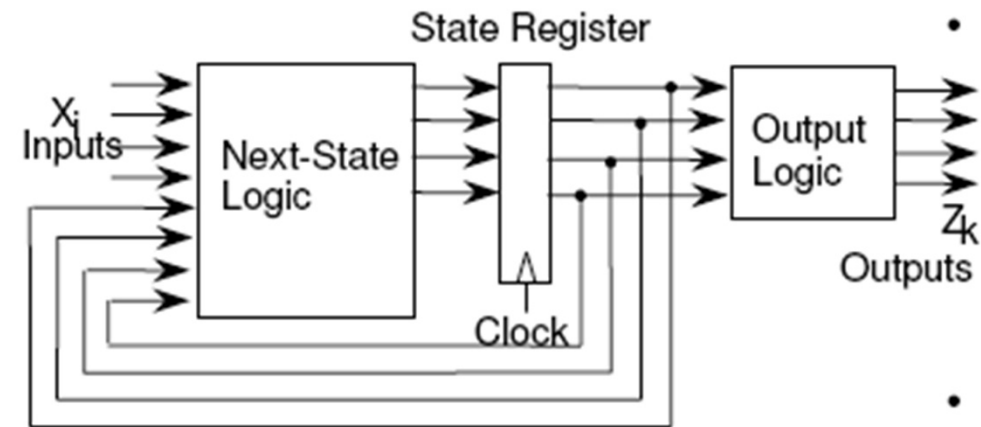

Moore Machine


The Example Vending Machine is a Moore Machine

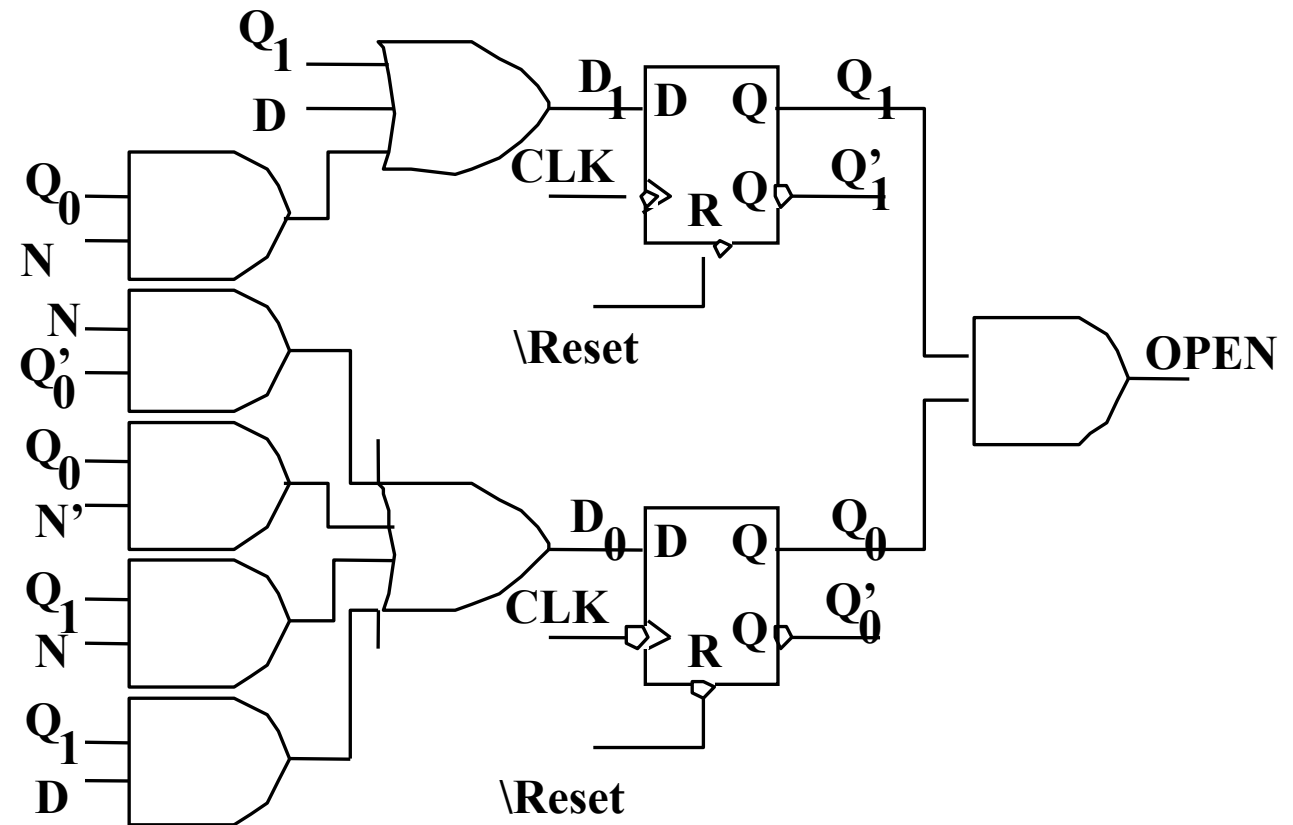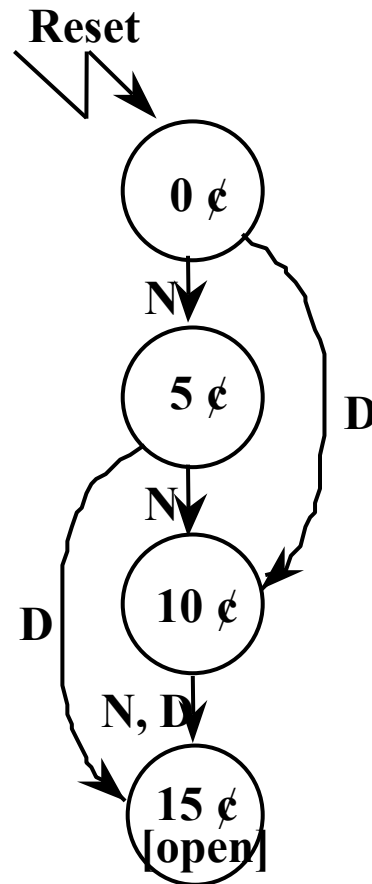- **Output is a function of the current states**
 - output is “in circle” in the state transition diagram
 - **Outputs change synchronously with states**



A Better Expression


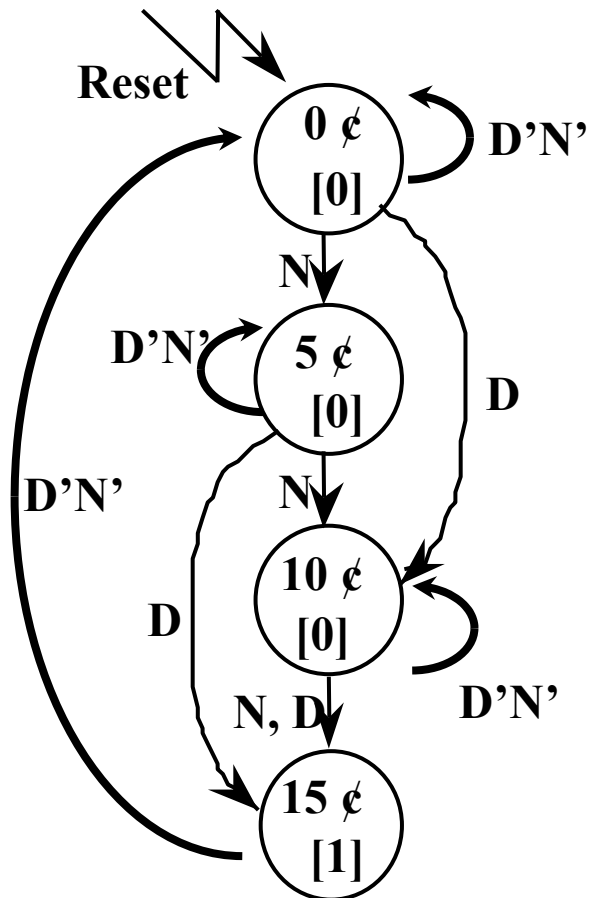
- Output is associated with current state in every circle
- After gum is released, 15 cents shall be transited to 0 cents



Present State	Inputs		Next State	Output Open
0 ¢	D	N	0 ¢	0
	0	1	5 ¢	0
	1	0	10 ¢	0
	1	1	X	X
5 ¢	0	0	5 ¢	0
	0	1	10 ¢	0
	1	0	15 ¢	0
	1	1	X	X
10 ¢	0	0	10 ¢	0
	0	1	15 ¢	0
	1	0	15 ¢	0
	1	1	X	X
15 ¢	0	0	0 ¢	1
	0	1	X	1
	1	0	X	1
	1	1	X	1


Transfer to the Mealy Machine

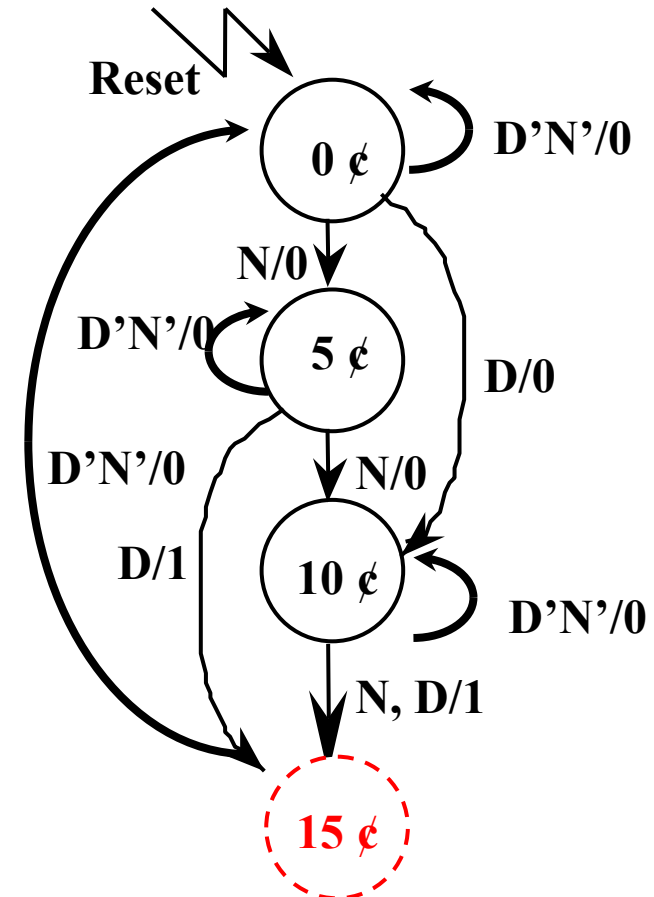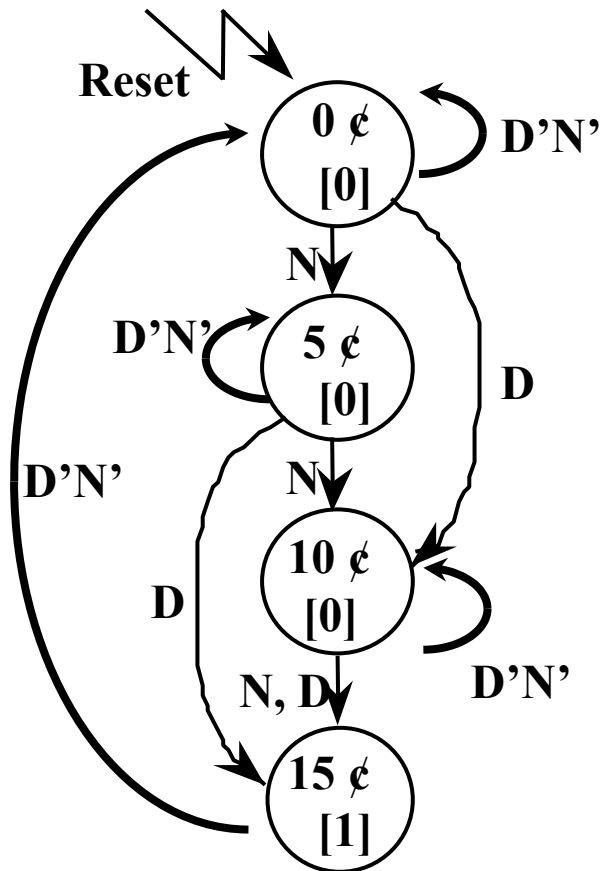- Transfer to Mealy machine by moving output to the branches
- Mealy machine tends to have fewer states
 - » Do we need state “15 cents”?



A Mealy Machine

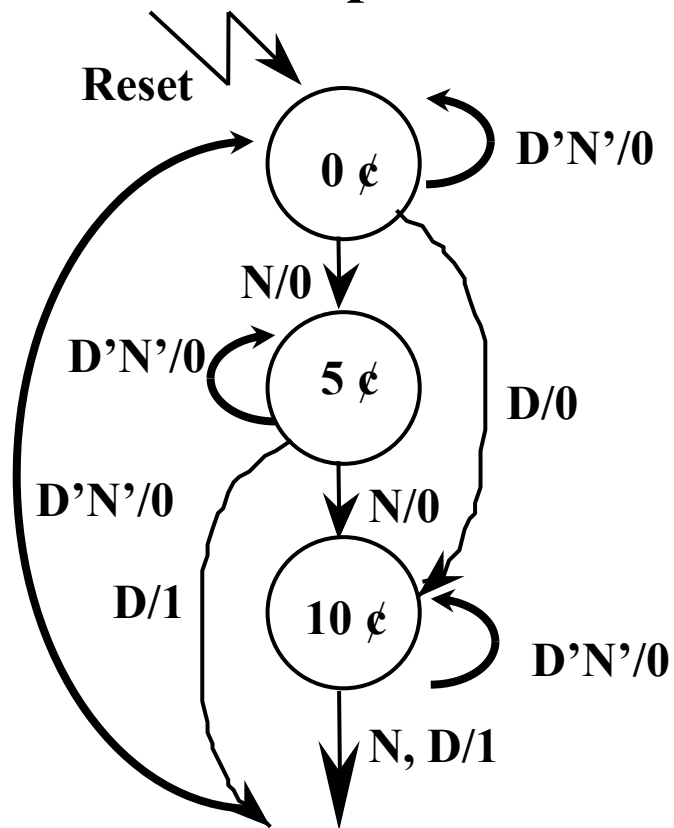- It really has fewer states than the Moore machine
 - » Use Mealy machine if it is not specified
 - » State “15 cents” can be combined with state “0 cents”
- Also note the output difference




Present State	Inputs D N		Next State	Output Open
0 ¢	0	0	0 ¢	0
	0	1	5 ¢	0
	1	0	10 ¢	0
	1	1	X	X
5 ¢	0	0	5 ¢	0
	0	1	10 ¢	0
	1	0	0 ¢	1
	1	1	X	X
10 ¢	0	0	10 ¢	0
	0	1	0 ¢	1
	1	0	0 ¢	1
	1	1	X	X



The D latch below is constructed with four NAND gates and an inverter. Consider the following three other ways for obtaining a D latch. In each case, draw the logic diagram and verify the circuit operation.



(a) Use NOR gates for the SR latch part and AND gates for the other two. An inverter may be needed.



(b) Use NOR gates for all four gates. Inverters may be needed.

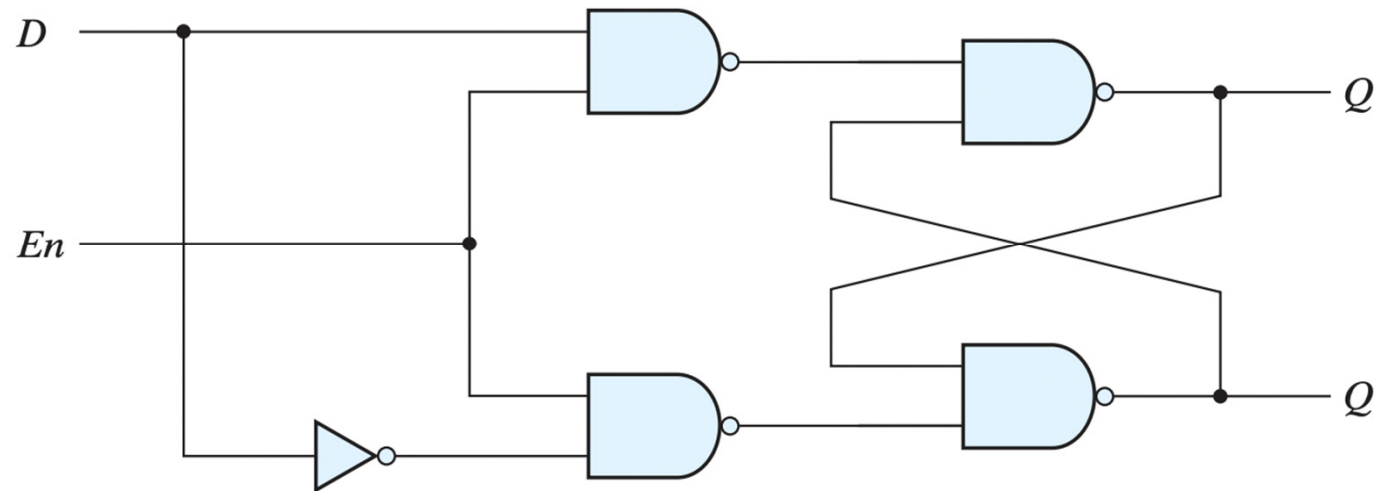(c) Use four NAND gates only (without an inverter). This can be done by connecting the output of the upper gate in below figure (the gate that goes to the SR latch) to the input of the lower gate (instead of the inverter output).



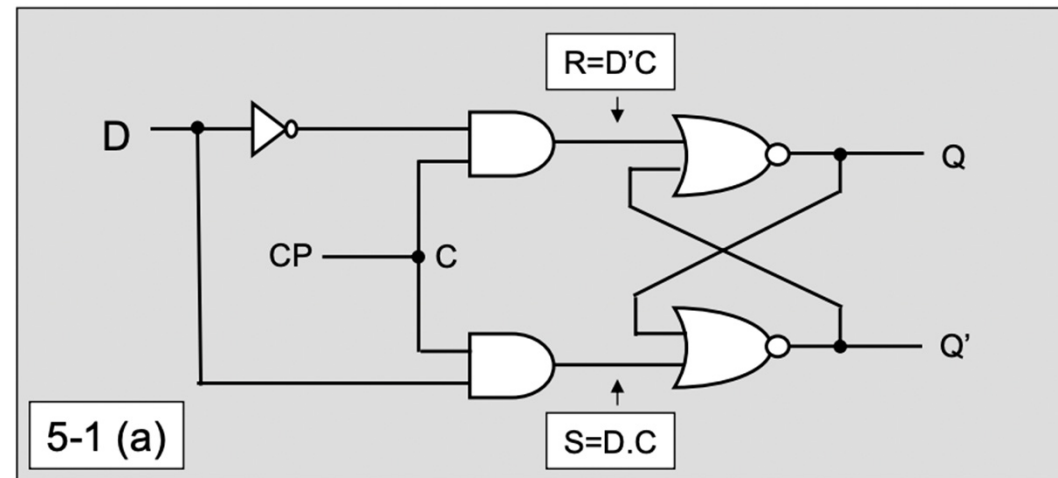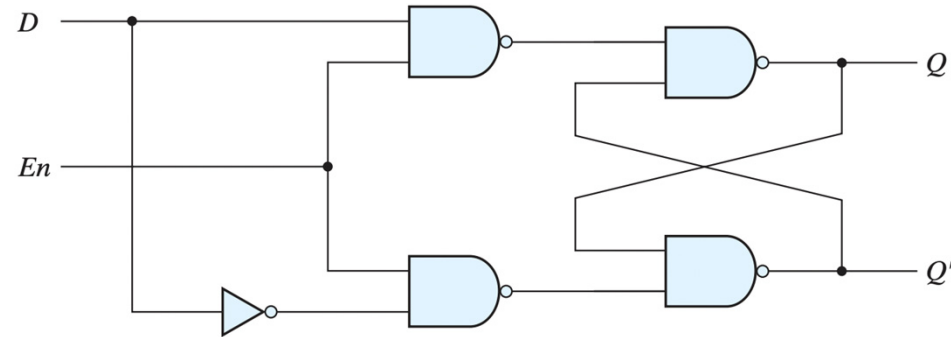

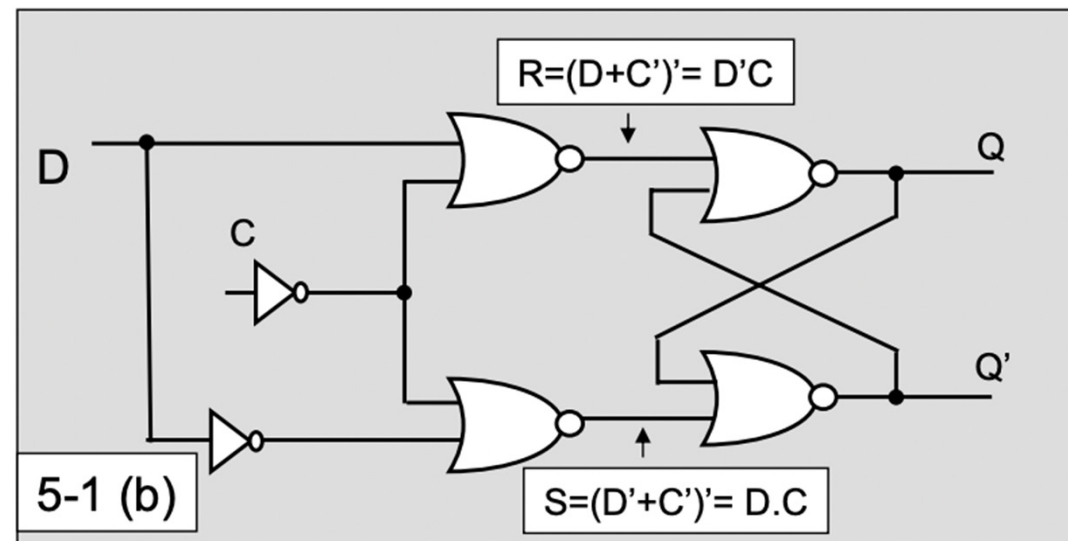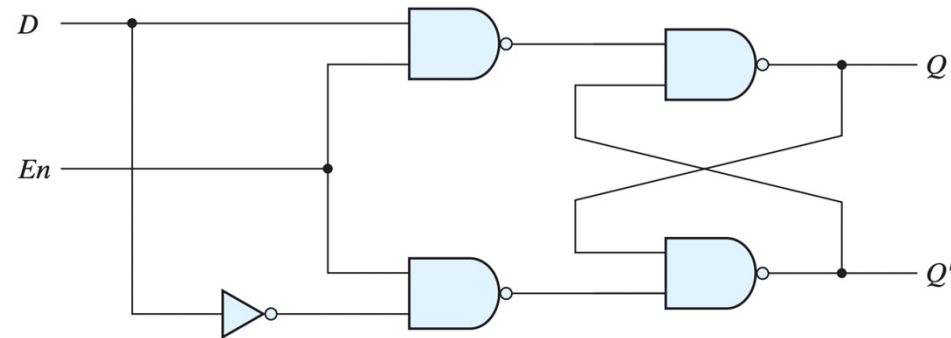

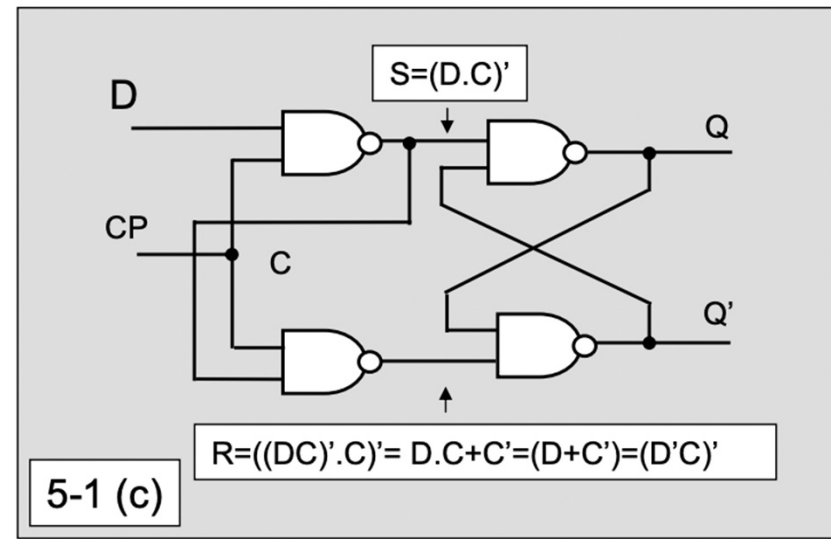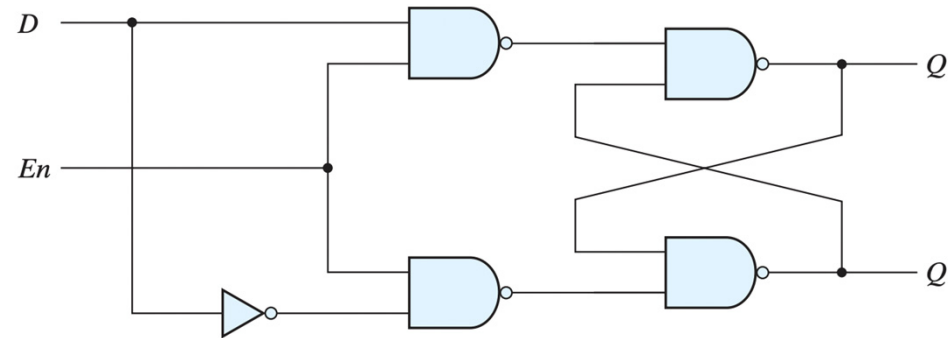

A PN flip-flop has four operations: clear to 0, no change, complement, and set to 1, when inputs P and N are 00, 01, 10, and 11, respectively.

- (a) Tabulate the characteristic table.**
- (b) Derive the characteristic equation.**
- (c) Tabulate the excitation table.**
- (d) Show how the PN flip-flop can be converted to a D flip-flop.**

P	N	Q(t)	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Q(t)	Q(t+1)	P	N
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1

5-4(d)	Connect P and N together
--------	--------------------------

Diagram illustrating a 2D array P with dimensions N (rows) and $Q(t)$ (columns). The array is shown as a grid of cells. Red brackets highlight the first column (index 1), the third column (index 1), and the fourth column (index 1).



香港科技大學
THE HONG KONG UNIVERSITY OF SCIENCE AND TECHNOLOGY

Thank you for listening !

